


EDA讲座2

主要内容

- ✓ 时序电路的FSM模型
- ✓ 时序always block
- ✓ 时序电路模块的HDL描述
- ✓ FSM的HDL描述
- ✓ EDA实验二内容

时序电路的FSM模型

 - Finite State Machines (FSMs) are a useful abstraction for sequential circuits with centralized “states” of operation
- At each clock edge, combinational logic computes *outputs* and *next state* as a function of *inputs* and *present state*



The Sequential always Block


- Edge-triggered circuits are described using a sequential always block

Combinational

```
module combinational(a, b, sel,
                    out);

    input a, b;
    input sel;
    output out;
    reg out;

     always @ (a or b or sel)
    begin
        if (sel) out = a;
        else out = b;
    end
endmodule
```




Sequential

```
module sequential(a, b, sel,
                 clk, out);

    input a, b;
    input sel, clk;
    output out;
    reg out;

 
    always @ (posedge clk)
    begin
        if (sel) out <= a;
        else out <= b;
    end
endmodule
```



非阻塞式赋值和阻塞式赋值


```
always @ (posedge clk)
begin
    q1 <= in;
    q2 <= q1;
    out <= q2;
end
```

 
“At each rising clock edge, $q1$, $q2$, and out **simultaneously receive the old values** of in , $q1$, and $q2$.”



```
always @ (posedge clk)
begin
    q1 = in;
    q2 = q1;
    out = q2;
end
```

 “At each rising clock edge, $q1 = in$.
After that, $q2 = q1 = in$.
After that, $out = q2 = q1 = in$.
Therefore $out = in$.”



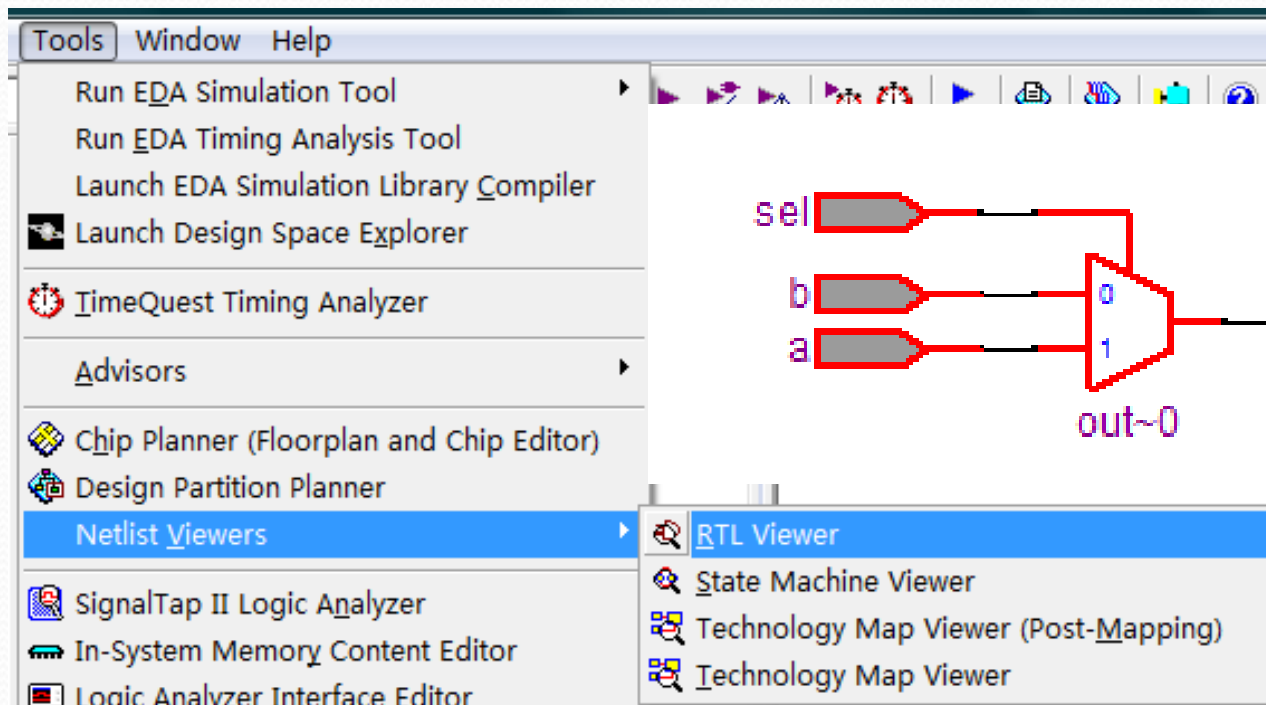


Combinational

```
module combinational(a, b, sel,
                    out);

    input a, b;
    input sel;
    output out;
    reg out;

     always @ (a or b or sel)
    begin
        if (sel) out = a;
        else out = b;
    end
endmodule
```




Sequential


```
module sequential(a, b, sel,
                 clk, out);

    input a, b;
    input sel, clk;
    output out;
    reg out;

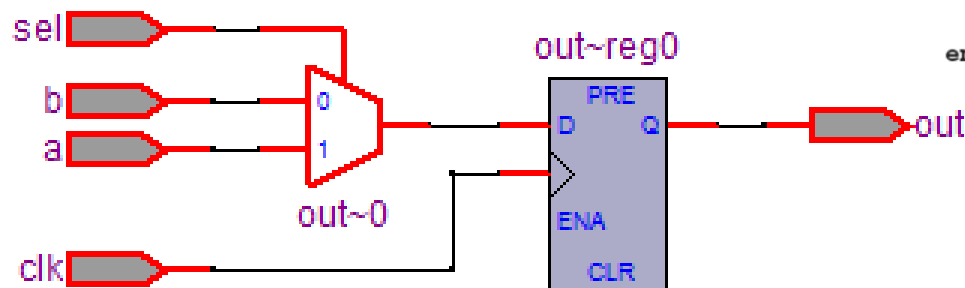    always @ (posedge clk)
    begin
        if (sel) out <= a;
        else out <= b;
    end
endmodule
```




非阻塞式赋值

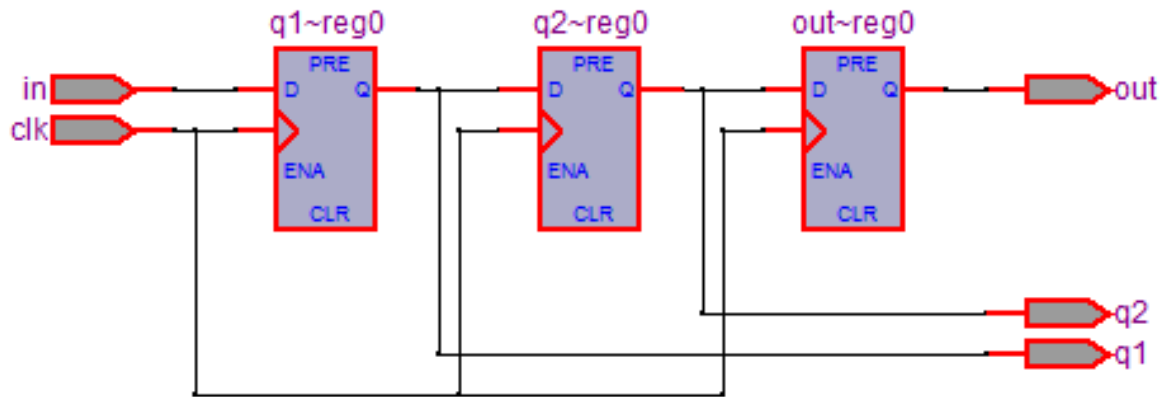

```
always @ (posedge clk)
begin
    q1 <= in;
    q2 <= q1;
    out <= q2;
end
```
 
```
always @ (posedge clk)
begin
    q1 = in;
    q2 = q1;
    out = q2;
end
```






阻塞式赋值

时序电路模块的HDL描述

D触发器
   
```
module d_ff(d,clk,q,qbar);  
    input d,clk;  
    output q,qbar;  
  
    reg q;  
  
    always @(posedge clk)  
    begin  
        q <= d;  
    end  
  
    assign qbar = ~q;  
  
endmodule
```





移位寄存器

```

module shift(mode,dir,dil,clk,d,q);
input [1:0]mode;
input dir,dil,clk;
input [3:0] d;
output [3:0]q;
reg [3:0]q;
always @(posedge clk)
begin
    case(mode)
        2'b00::
        2'b01:begin q <={q[2:0],dir}; end
        2'b10:begin q <={dil,q[3:1]}; end
        2'b11:begin q <=d; end
    endcase
end
endmodule

```

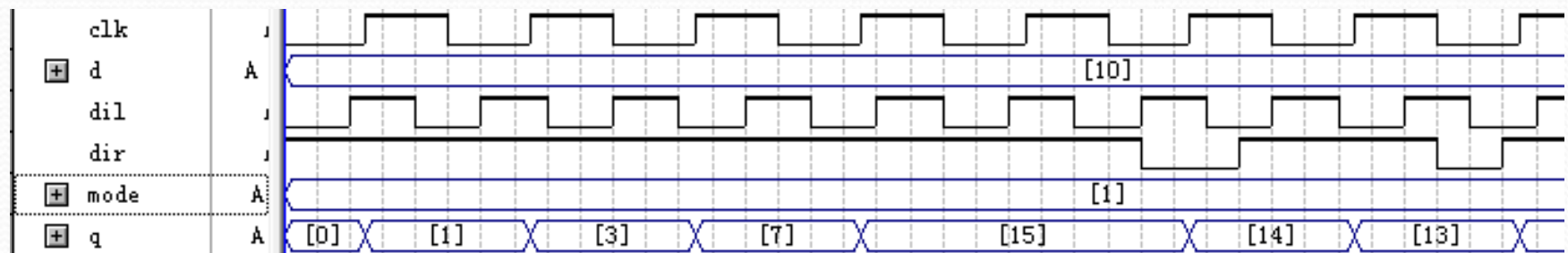 


计数器 (74163)

```
module counter(LDbar, CLRbar, P, T, CLK, D,
               count, RCO);
    input LDbar, CLRbar, P, T, CLK;
    input [3:0] D;
    output [3:0] count;
    output RCO;
    reg [3:0] Q;
```



```
    always @ (posedge CLK) begin
        if (!CLRbar) Q <= 4'b0000;
        else if (!LDbar) Q <= D;
        else if (P && T) Q <= Q + 1;
    end
```

```
    assign count = Q;
    assign RCO = Q[3] & Q[2] & Q[1] & Q[0] & T;
endmodule
```

priority logic for
control signals

 


RCO gated
by T input

 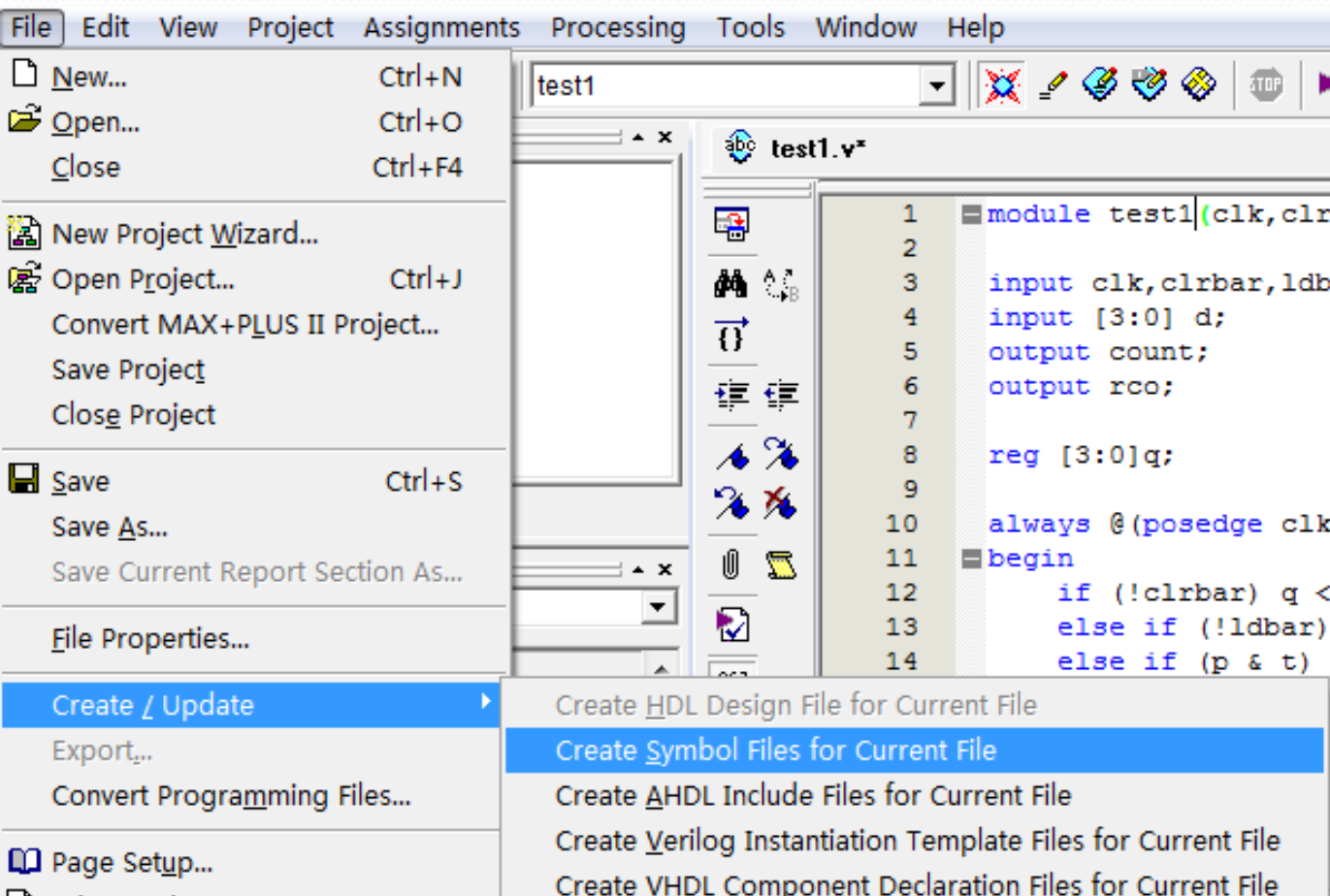

FSM的HDL描述

 - Finite State Machines (FSMs) are a useful abstraction for sequential circuits with centralized “states” of operation
- At each clock edge, combinational logic computes *outputs* and *next state* as a function of *inputs* and *present state*







```




module mylock(clk,key,reset,unlock);
    input clk, key, reset;
    output reg unlock;
    reg [1:0]state;

    parameter S0 = 0, S1 = 1, S2 = 2, S3 = 3;
    always @ (posedge clk or posedge reset) begin
        if (reset) begin state <= S0; unlock <= 0;end
        else
            case (state)
                S0:
                    if (key) begin state <= S1;unlock <= 0;end
                    else begin state <= S0;unlock <= 0;end
                S1:
                    if (key) begin state <= S2;unlock <= 0;end
                    else begin state <= S0;unlock <= 0;end
                S2:
                    if (key) begin state <= S2;unlock <= 1;end
                    else begin state <= S0;unlock <= 0;end
                S3:
                    if (key) begin state <= S1;unlock <= 0;end
                    else begin state <= S1;unlock <= 0;end
            endcase
        end
    end
endmodule

```

  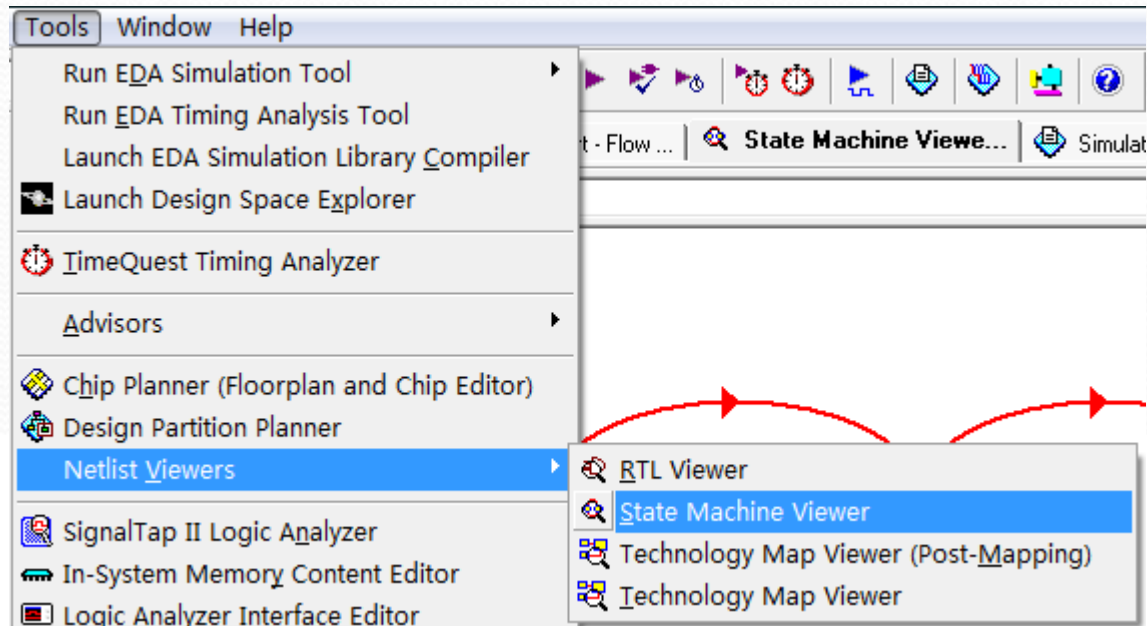




 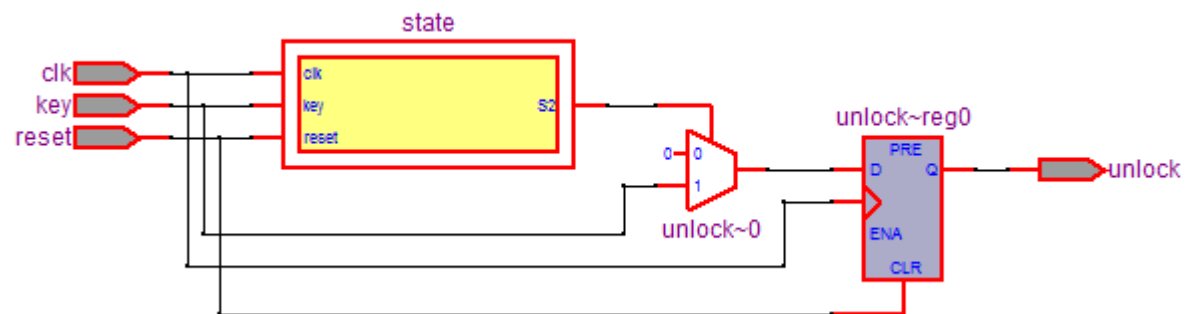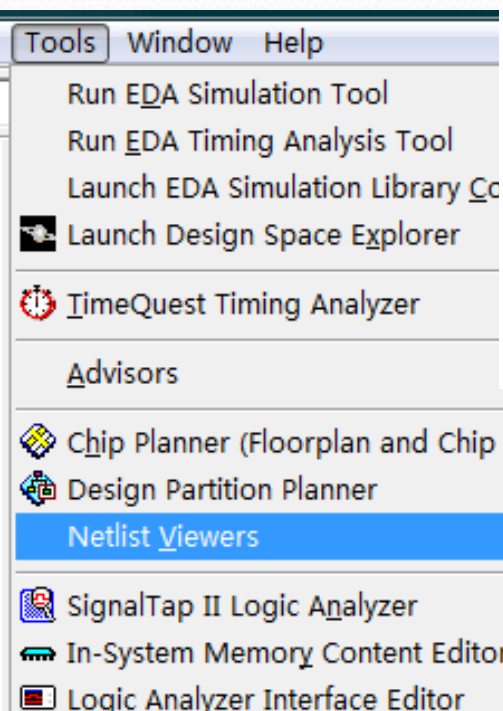


```

always @(state or key or reset)
begin
    if (reset)    unlock <= 0;
    else unlock <= (state == S2) && (key == 1);
end

```

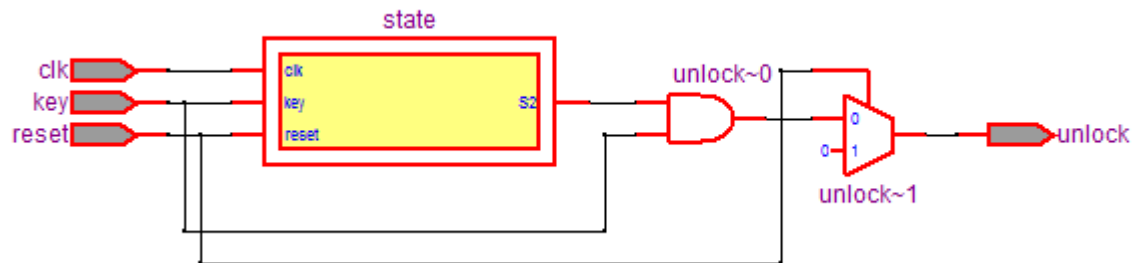


clk
 reset
 key
 unlock

 


```
always @ (posedge clk)
    begin cur_state <= next_state; end
```

```
always @ (cur_state or reset or key) begin
    if (reset) begin next_state <= S0; end
    else
        case (cur_state)
            S0: next_state <= ...;
            S1: ...
        endcase
    end
end
```
 
```
always @ (cur_state or reset or key)
    begin
        if (reset) unlock <= 0;
        else unlock <= (cur_state == S2) && (key == 1);
    end
```






EDA实验二内容

Vending machine

利用实验板上的拨码开关和按键开关模拟**投币**、**购物**和**退币**输入，用**发光二极管**模拟各种提示信息，用**数码管**显示余额，实现一个自动售货机内部控制电路。要求满足如下规格：

 - 1) 可接受**5角**、**1元**和**5元**的投币，每次购买允许投入多种不同币值的钱币；用**3只数码管**显示当前投币金额，如055表示已投币5.5元；
- 2) 可售出价格分别为**1.5元**和**2.5元**的商品，假设用户每次购买时只选择单件、一种商品；允许用户多次购买商品，每次购买后，可以进行补充投币；
- 3) 选择购买商品后，如果投币**金额不足**，则提醒；否则，售出相应的商品，并提醒用户取走商品；
- 4) 若用户选择**退币**，则退回余下的钱，并提醒用户取钱。



实验板上有40MHz的时钟信号，对应FPGA引脚号为PIN_152，自动售货机的工作时钟及数码管循环扫描显示的时钟可由该40MHz分频得到。

